

PLL Design and Simulation by Dean Banerjee

ENTER THESE (yellow)...

$\phi := 50 \cdot \text{deg}$	Phase margin. Default is 50 degrees.
$F_c := 100 \cdot \text{kHz}$	Loop Bandwidth.
$F_{\text{comp}} := 16 \cdot \text{MHz}$	Comparison Frequency
$K_{\text{vco}} := 40 \cdot \frac{\text{MHz}}{\text{volt}}$	VCO Tuning Constant
$K_{\phi} := 30 \cdot \mu\text{A}$	Phase Detector gain do not divide by $2 \cdot \pi$
$F_{\text{out}} := 1760 \cdot \text{MHz}$	RF output frequency. Choose equal to $\sqrt{F_{\text{max}} \cdot F_{\text{min}}}$
$T_3 T_1 := 29$ %	Ratio of Poles T_3/T_1 expressed as a percentage. Choose from 0 to 100. 0 = second order filter. Default is 50%
$\text{method} := 1$	Set method = 0 to use a more standard set of design equations. Set method = 1 to use the Ultimate method, which is unorthodox, but does not use any approximations

CALCULATIONS USING THE ULTIMATE METHOD

$$N := \frac{F_{\text{out}}}{F_{\text{comp}}} \quad \phi_c := 2 \cdot \pi \cdot F_c$$

SOLVE FOR T1 AND T2

$$f(x) := \frac{x}{1+x^2} + \frac{x \cdot \frac{T_3 T_1}{100}}{1 + \left(x \cdot \frac{T_3 T_1}{100} \right)^2} \quad g(x) := \frac{1 + \sqrt{1 - 4 \cdot f(x)^2}}{2 \cdot f(x)}$$

This finds $\omega_c T_2$ as a function of $\omega_c T_1$ (or x)

$$x := 3 \cdot 10^{-5}$$

$$T_1 := \frac{\text{root} \left[g(x) - x \cdot g(x) \cdot x \cdot \frac{T_3 T_1}{100} - x - x \cdot \frac{T_3 T_1}{100} - \tan(\phi) \left[1 - x \cdot x \cdot \frac{T_3 T_1}{100} + g(x) \cdot \left(x + x \cdot \frac{T_3 T_1}{100} \right) \right], x \right]}{\phi_c}$$

$$T_2 := \frac{g(\phi_c \cdot T_1)}{\phi_c}$$

$$T_3 := \frac{T_3 T_1}{100} \cdot T_1$$

$$T_1 = 4.277 \times 10^{-7} \text{ s}$$

$$T_2 = 4.256 \times 10^{-6} \text{ s}$$

$$T_3 = 1.24 \times 10^{-7} \text{ s}$$

SET UP SYSTEM OF 4 EQUATIONS AND 4 UNKNOWNNS

$$k_1 := \left(\frac{K? \cdot K_{vco}}{N} \right) \cdot \sqrt{\frac{1 + (?c \cdot T_2)^2}{[1 + (?c \cdot T_1)^2] \cdot [1 + (?c \cdot T_3)^2]}} \cdot \frac{1}{?c^2}$$

$$k_1 = 0.076 \cdot nF$$

$$k_2 := (T_1 + T_3) \cdot k_1$$

$$k_2 = 4.191 \times 10^{-8} \cdot \text{sec} \cdot nF$$

$$k_3 := \frac{T_3 \cdot T_1 \cdot k_1}{T_2}$$

$$k_3 = 9.467 \times 10^{-10} \cdot \text{sec} \cdot nF$$

USE THESE EQUATIONS TO FIND THE MAXIMUM VALUE FOR k4

$$A := k_3^2$$

$$A = 0 \cdot \text{sec}^2 \cdot nF^2$$

$$B := 2 \cdot k_2 \cdot k_3 - 4 \cdot T_2 \cdot k_1 \cdot k_3$$

$$B = -1.145 \times 10^{-15} \cdot \text{sec}^2 \cdot nF$$

$$C := k_2^2 - 4 \cdot T_2 \cdot k_3 \cdot k_1$$

$$C = 0 \cdot \text{sec}^2 \cdot nF^2$$

$$k_{4\min} := \frac{-B - \sqrt{B^2 - 4 \cdot A \cdot C}}{2 \cdot A}$$

$$k_{4\min} = 0.465$$

$$k_{4\max} := \frac{-B + \sqrt{B^2 - 4 \cdot A \cdot C}}{2 \cdot A}$$

$$k_{4\max} = 1.277 \times 10^{-1} \quad k_4 := k_{4\min}$$

NOW SOLVE FOR C1 AND THE OTHER COMPONENTS

$$A := T_2 \cdot (k_4 + 1)$$

$$A = 6.234 \times 10^{-6} \text{ s}$$

$$B := -k_2 - k_3 \cdot k_4$$

$$B = -4.235 \times 10^{-5} \cdot \text{sec} \cdot pF$$

$$C := k_3 \cdot k_1$$

$$C = 7.191 \times 10^{-5} \cdot \text{sec} \cdot pF^2$$

SOLVE FOR COMPONENTS

$$C_1 := \frac{-B}{2 \cdot A}$$

$$C_3 := k_4 \cdot C_1$$

$$C_2 := k_1 - C_3 - C_1$$

$$R_3 := \frac{k_3}{C_1 \cdot C_3}$$

$$R_2 := \frac{T_2}{C_2}$$

CALCULATIONS USING THE STANDARD METHOD

$$T_1 := \frac{\left(\frac{1}{\cos(?)} \right) - \tan(?)}{?c \cdot \left(\frac{T_3 T_1}{100} + 1 \right)}$$

$$T_3 := \frac{T_3 T_1}{100} \cdot T_1$$

$$T_2 := \frac{1}{[?c^2 \cdot (T_1 + T_3)]}$$

$$C1s := \frac{T1}{T2} \cdot \frac{K? \cdot Kvco}{? c^2 \cdot N} \cdot \left[\frac{1 + ? c^2 \cdot T2^2}{(1 + ? c^2 \cdot T1^2) \cdot (1 + ? c^2 \cdot T3^2)} \right]^{\frac{1}{2}}$$

$$C2s := C1s \cdot \left(\frac{T2}{T1} - 1 \right)$$

$$C3s := \frac{C1s}{10}$$

$$R2s := \frac{T2}{C2s}$$

$$R3s := \frac{T3}{C3s}$$

ASSIGN COMPONENT VALUES BASED ON USER'S SELECTION OF EITHER THE STANDARD OR ULTIMATE METHOD

$$\underline{C1} := \text{if}(\text{method} > 0.5, C1, C1s) \quad \underline{C3} := \text{if}(\text{method} > 0.5, C3, C3s) \quad \underline{R3} := \text{if}(\text{method} > 0.5, R3, R3s)$$

$$\underline{C2} := \text{if}(\text{method} > 0.5, C2, C2s) \quad \underline{R2} := \text{if}(\text{method} > 0.5, R2, R2s)$$

THE CALCULATED VALUES ARE SHOWN BELOW

$$C1 = 3.3961495 \cdot \text{pF}$$

$$C2 = 70.985 \cdot \text{pF}$$

$$C3 = 1.5787201 \cdot \text{pF}$$

$$R2 = 59.9571793 \cdot \text{k}\Omega$$


$$R3 = 176.5631296 \cdot \text{k}\Omega$$

ENTER PARAMETERS HERE

$$K? := K? \quad F_{\text{comp}} := F_{\text{comp}} \quad F_{\text{out}} := F_{\text{out}} \quad Kvco := Kvco$$

$$C1 := C1 \quad R3 := R3 \quad C2 := C2 \quad C3 := C3 \quad R2 := R2$$

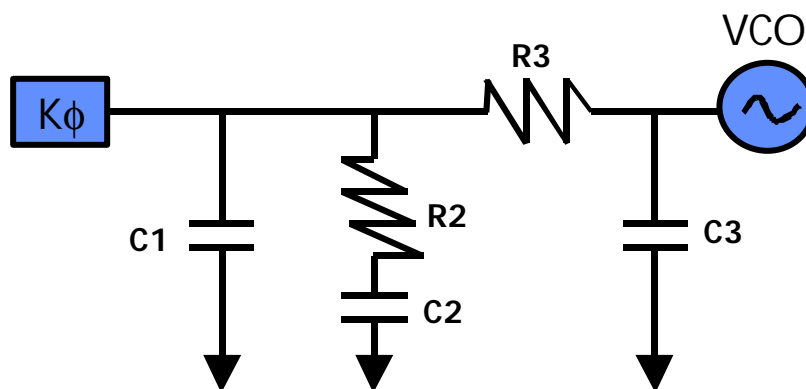Changes to actual loop filter: $\underline{C3} := 3\text{pF}$



CALCULATE PARAMETERS

$$N := \frac{F_{out}}{F_{comp}}$$

$$? := \frac{R2 \cdot C2}{2} \cdot \sqrt{\frac{K? \cdot K_{vco}}{N \cdot (C1 + C2 + C3)}}$$

$$?n := \sqrt{\frac{K? \cdot K_{vco}}{N \cdot (C1 + C2 + C3)}}$$

$$N = 110$$

$$? = 0.799$$

$$\frac{?n}{2 \cdot p} = 59.758 \cdot \text{kHz}$$

CALCULATE THE TRUE POLES AND ZERO

$$T2 := R2 \cdot C2$$

$$x := \frac{C2 \cdot C3 \cdot R2 + C1 \cdot C2 \cdot R2 + C1 \cdot C3 \cdot R3 + C2 \cdot C3 \cdot R3}{C1 + C2 + C3}$$

This is T1+T3

$$y := \frac{R2 \cdot R3 \cdot C1 \cdot C2 \cdot C3}{C1 + C2 + C3}$$

This is T1*T3

$$T1 := \frac{x + \sqrt{x^2 - 4 \cdot y}}{2}$$

$$T3 := \frac{x - \sqrt{x^2 - 4 \cdot y}}{2}$$

junk := T3

Make sure that T1 and T3 are not switched

$$T3 := \text{if}(T3 > T1, T1, T3)$$

$$T1 := \text{if}(T3 > T1, \text{junk}, T1)$$

Time Constant

Filter Pole

Filter Zero

$$T1 = 7.244 \times 10^{-7} \text{ s}$$

$$\frac{1}{T1} = 1.381 \times 10^3 \cdot \text{kHz}$$

n/a

$$T2 = 4.256 \times 10^{-6} \text{ s}$$

n/a

$$\frac{1}{T2} = 234.96 \cdot \text{kHz}$$

$$T3 = 1.366 \times 10^{-7} \text{ s}$$

$$\frac{T3}{T1} = 18.857 \cdot \%$$

$$\frac{1}{T3} = 7.321 \times 10^3 \cdot \text{kHz}$$

n/a

DEFINE LOOP PARAMETERS

$$Z(?) := \frac{1 + T2 \cdot i \cdot ?}{i \cdot ? \cdot (C1 + C2 + C3) \cdot (1 + i \cdot ? \cdot T1) \cdot (1 + i \cdot ? \cdot T3)}$$

Loop Filter Impedance


$$G(?) := \frac{K? \cdot K_{vco} \cdot Z(?)}{i \cdot ?}$$

Forward Loop Gain

$$CL(?) := \frac{G(?)}{1 + \frac{G(?)}{N}}$$

Closed Loop Gain
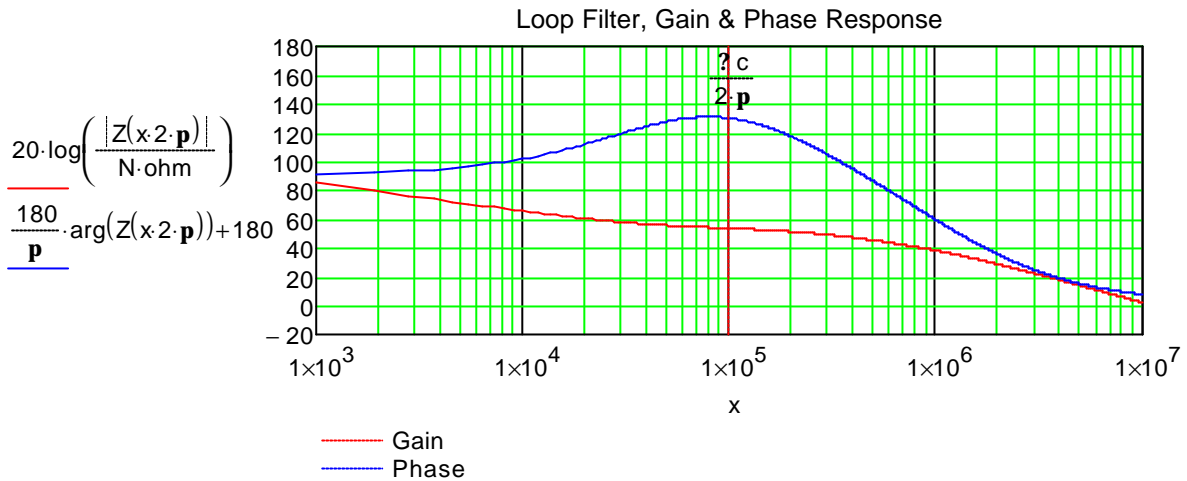
$$x := 100 \cdot \text{Hz}, 1000 \cdot \text{Hz} \dots \frac{100 \cdot ? \cdot c}{2 \cdot p}$$



BANDWIDTH AND PHASE MARGIN

$$? := 600.0 \cdot \text{kHz}$$

Initial Guess for Loop Bandwidth

$$? c := \text{root}(|G(?)| - N, ?)$$

$$\frac{? c}{2 \cdot \mathbf{p}} = 94.142 \cdot \text{kHz}$$

Loop Bandwidth

$$? := ? c$$

$$\frac{\text{root}(|CL(?)| - N, ?)}{2 \cdot \mathbf{p}} = 135.097 \cdot \text{kHz}$$

0 db Bandwidth

$$\frac{\text{root}\left(|CL(?)| - \frac{N}{\sqrt{2}}, ?\right)}{2 \cdot \mathbf{p}} = 166.638 \cdot \text{kHz}$$

3 db Bandwidth

$$\arg(G(? c)) \cdot \frac{180}{\mathbf{p}} + 180 = 40.523$$

Phase Margin

ADDED SPURIOUS ATTENUATION (THIRD ORDER FILTERS ONLY)

$$\text{spur}(?) := 10 \cdot \log\left[\frac{1 + [? c \cdot (T1 + T3)]^2}{1 + [? \cdot (T1 + T3)]^2} \cdot \frac{1 + (? \cdot T1)^2}{1 + (? c \cdot T1)^2} \cdot \frac{1 + (? \cdot T3)^2}{1 + (? c \cdot T3)^2}\right]$$

$$\text{spur}(2 \cdot \mathbf{p} \cdot \text{Fcomp}) = 21.518$$

Additional Reference freq (Fc) Atteunation

$$\text{spur}\left(\frac{1}{4} \cdot 2 \cdot \mathbf{p} \cdot \text{Fcomp}\right) = 9.812$$

Attenuation at Fc/4

OPTIMIZATION INDEX (100% = Most Optimized)


$$\text{Index} := \frac{\frac{T2}{1 + (? c \cdot T2)^2}}{\frac{T1}{1 + (? c \cdot T1)^2} + \frac{T3}{1 + (? c \cdot T3)^2}}$$

$$\text{Index} := \text{if}\left(\text{Index} > 1, \frac{1}{\text{Index}}, \text{Index}\right)$$

$$\text{Index} = 77.572 \cdot \%$$

This is the Optimization Index in Percent

DISPLAY BODE PLOT

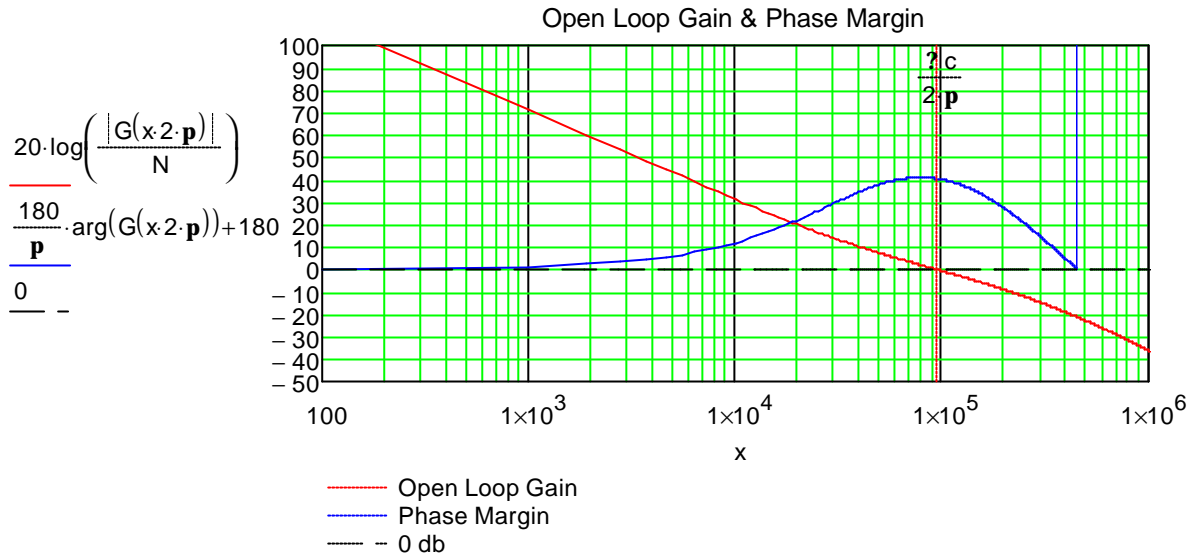

PHASE NOISE PROFILE FOR A NOISELESS VCO

Noise1Hz := -202

dbc/Hz

1 Hz Normalized Phase Detector
Phase Noise, max typically -207

$$\text{NoiseFloor} := \text{Noise1Hz} + 10 \cdot \log\left(\frac{F_{\text{comp}}}{\text{Hz}}\right)$$

NoiseFloor = -129.959

dbc/Hz

Noise Floor of PLL (in loop)


NoiseFloor + 20 · log(N) = -89.131

dbc/Hz

In loop Phase Noise

$$\sqrt{\frac{2 \cdot \text{sec}}{p}} \int_{10 \cdot \text{Hz}}^{4 \cdot c} \frac{\text{NoiseFloor}}{10^{10}} \cdot (|CL(?)|)^2 d? = 2.114 \cdot \text{deg}$$

RMS Phase Error

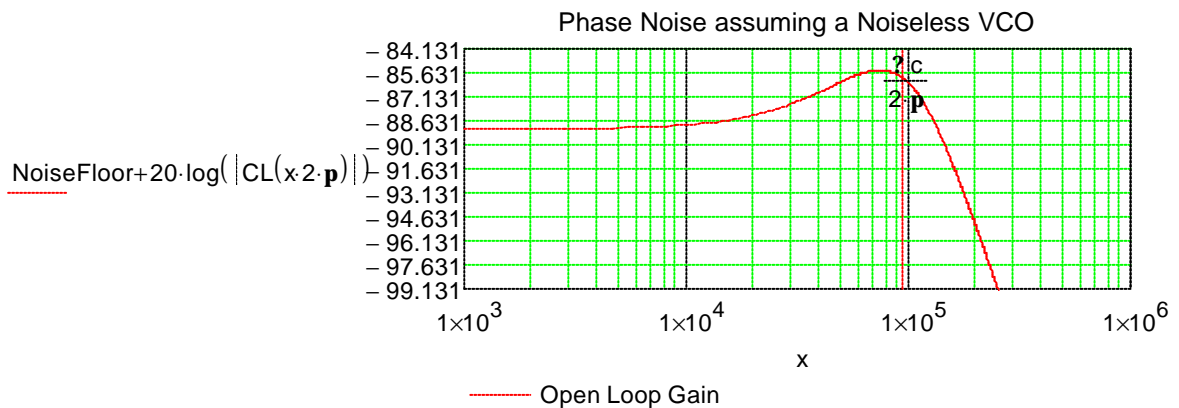

TRANSIENT ANALYSIS

f2 := 1760·MHz

Final Frequency

f1 := 1860·MHz

Starting Frequency

$$R3 := \max\left(\begin{pmatrix} R3 \\ 1 \cdot \mathbf{0} \end{pmatrix}\right) \quad C3 := \max\left(\begin{pmatrix} C3 \\ 1 \cdot \text{pF} \end{pmatrix}\right)$$

$$N := \frac{f2}{F_{\text{comp}}} \quad \text{den2} := C1 + C2 + C3 \quad \text{den3} := C2 \cdot C3 \cdot R2 + C1 \cdot C2 \cdot R2 + C1 \cdot C3 \cdot R3 + C2 \cdot C3 \cdot R3$$

$$\text{den4} := R2 \cdot R3 \cdot C1 \cdot C2 \cdot C3$$

$$\text{den1} := \frac{K? \cdot K_{\text{vco}} \cdot C2 \cdot R2}{N} \quad \text{num0} := \frac{K? \cdot K_{\text{vco}} \cdot (f2 - f1)}{N}$$

$$\text{den0} := \frac{K? \cdot K_{\text{vco}}}{N} \quad \text{num1} := \text{num0} \cdot R2 \cdot C2$$

$$v := \begin{pmatrix} \frac{\text{den0}}{\text{den4}} \cdot \text{sec}^4 \\ \frac{\text{den1}}{\text{den4}} \cdot \text{sec}^3 \\ \frac{\text{den2}}{\text{den4}} \cdot \text{sec}^2 \\ \frac{\text{den3}}{\text{den4}} \cdot \text{sec} \\ 1 \end{pmatrix} \quad v = \begin{pmatrix} 1.425 \times 10^{24} \\ 6.064 \times 10^{18} \\ 1.011 \times 10^{13} \\ 8.702 \times 10^6 \\ 1 \end{pmatrix}$$

$$p := \text{polyroots}(v) \cdot \text{sec}^{-1} \quad p = \begin{pmatrix} -7.451 \times 10^6 \\ -4.451 \times 10^5 \\ -4.028 \times 10^5 - 5.171i \times 10^5 \\ -4.028 \times 10^5 + 5.171i \times 10^5 \end{pmatrix} \text{s}^{-1} \quad \text{These are the poles}$$

$$A_0 := \frac{\text{num0}}{\text{den4} \cdot (p_0 - p_1) \cdot (p_0 - p_2) \cdot (p_0 - p_3)}$$

$$A_0 = 4.072 \times 10^{11} \text{s}^{-2}$$

$$A_1 := \frac{\text{num0}}{\text{den4} \cdot (p_1 - p_0) \cdot (p_1 - p_2) \cdot (p_1 - p_3)}$$

$$A_1 = -7.555 \times 10^{13} \text{s}^{-2}$$

$$A_2 := \frac{\text{num0}}{\text{den4} \cdot (p_2 - p_0) \cdot (p_2 - p_1) \cdot (p_2 - p_3)}$$

$$A_2 = (3.757 \times 10^{13} - 3.103i \times 10^{11}) \text{s}^{-2}$$

$$A_3 := \frac{\text{num0}}{\text{den4} \cdot (p_3 - p_0) \cdot (p_3 - p_1) \cdot (p_3 - p_2)}$$

$$A_3 = (3.757 \times 10^{13} + 3.103i \times 10^{11}) \text{s}^{-2}$$

4 Pole Analysis

$k := 0..4000$ $i := 0..3$

$$t_k := \frac{k}{10000000} \cdot \text{sec} \quad F(t, k) := f_2 + \sum_i \left[A_i \cdot e^{(p_i \cdot t_k)} \cdot \left(\frac{1}{p_i} + R_2 \cdot C_2 \right) \right]$$

$\text{range} := 100 \cdot 10^{(-6)} \cdot \text{sec}$

Maximum Range of the X axis

$\text{tol} := -0.01 \cdot \text{MHz}$


Tolerance Marker for Lock Time Measurements

$\text{span} := 200 \cdot \text{MHz}$

Vertical Span of the Plot

$\text{center} := 1760 \cdot \text{MHz}$

Center Frequency

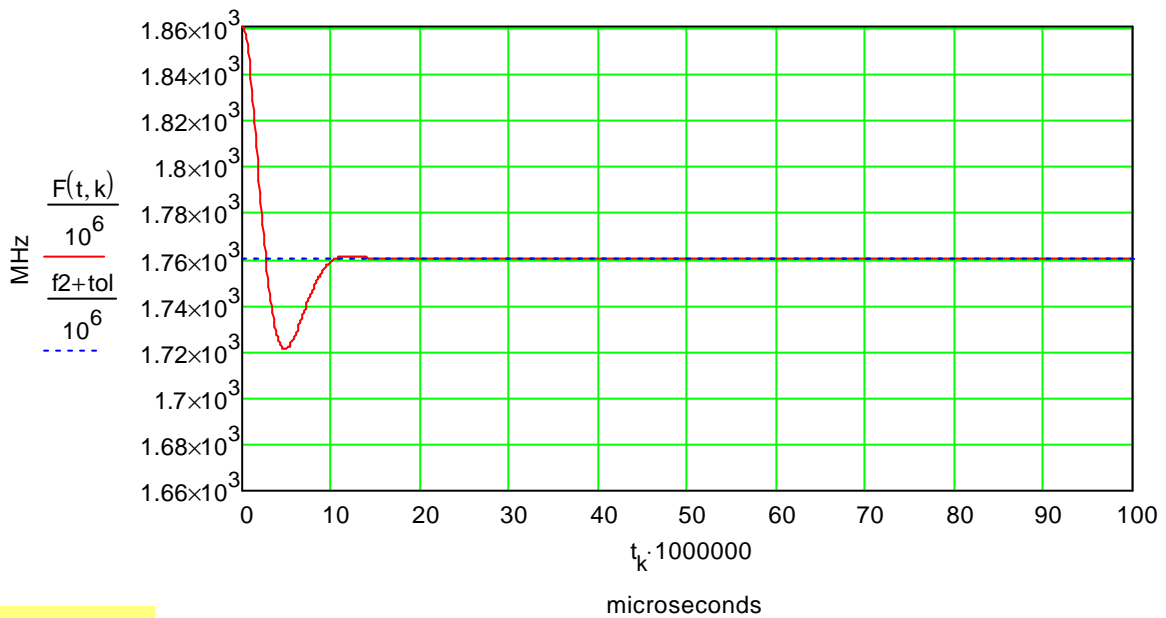

$\text{span} := 0.2 \cdot \text{MHz}$

