

PLL Design and Simulation by Dean Banerjee

ENTER THESE (yellow)...

| | |
|---|---|
| $\phi := 50 \cdot \text{deg}$ | Phase margin. Default is 50 degrees. |
| $F_c := 100 \cdot \text{kHz}$ | Loop Bandwidth. |
| $F_{\text{comp}} := 16 \cdot \text{MHz}$ | Comparison Frequency |
| $K_{\text{vco}} := 40 \cdot \frac{\text{MHz}}{\text{volt}}$ | VCO Tuning Constant |
| $K_{\phi} := 30 \cdot \mu\text{A}$ | Phase Detector gain do not divide by $2 \cdot \pi$ |
| $F_{\text{out}} := 1760 \cdot \text{MHz}$ | RF output frequency. Choose equal to $\text{sqrt}(F_{\text{max}} \cdot F_{\text{min}})$ |
| $T3T1 := 29$ % | Ratio of Poles T3/T1 expressed as a percentage. Choose from 0 to 100. 0 = second order filter. Default is 50% |
| $\text{method} := 1$ | Set method = 0 to use a more standard set of design equations. Set method = 1 to use the Ultimate method, which is unorthodox, but does not use any approximations |

CALCULATIONS USING THE ULTIMATE METHOD

$$N := \frac{F_{\text{out}}}{F_{\text{comp}}} \qquad \omega_c := 2 \cdot \pi \cdot F_c$$

SOLVE FOR T1 AND T2

$$f(x) := \frac{x}{1+x^2} + \frac{x \cdot \frac{T3T1}{100}}{1 + \left(x \cdot \frac{T3T1}{100}\right)^2} \qquad g(x) := \frac{1 + \sqrt{1 - 4 \cdot f(x)^2}}{2 \cdot f(x)}$$

This finds $\omega_c T2$ as a function of $\omega_c T1$ (or x)

$$x := 3 \cdot 10^{-5}$$

$$T1 := \frac{\text{root} \left[g(x) - x \cdot g(x) \cdot x \cdot \frac{T3T1}{100} - x - x \cdot \frac{T3T1}{100} - \tan(\phi) \left[1 - x \cdot x \cdot \frac{T3T1}{100} + g(x) \cdot \left(x + x \cdot \frac{T3T1}{100} \right) \right], x \right]}{\omega_c}$$

$$T2 := \frac{g(\omega_c \cdot T1)}{\omega_c}$$

$$T3 := \frac{T3T1}{100} \cdot T1$$

$$T1 = 4.277 \times 10^{-7} \text{ sec}$$

$$T2 = 4.256 \times 10^{-6} \text{ sec}$$

$$T3 = 1.24 \times 10^{-7} \text{ sec}$$

SET UP SYSTEM OF 4 EQUATIONS AND 4 UNKNOWNNS

$$k1 := \left(\frac{K\phi \cdot Kvco}{N} \right) \cdot \sqrt{\frac{1 + (\omega c \cdot T2)^2}{[1 + (\omega c \cdot T1)^2] \cdot [1 + (\omega c \cdot T3)^2]}} \cdot \frac{1}{\omega c^2} \quad k1 = 0.076 \text{ nF}$$

$$k2 := (T1 + T3) \cdot k1 \quad k2 = 4.191 \times 10^{-8} \text{ sec} \cdot \text{nF}$$

$$k3 := \frac{T3 \cdot T1 \cdot k1}{T2} \quad k3 = 9.467 \times 10^{-10} \text{ sec} \cdot \text{nF}$$

USE THESE EQUATIONS TO FIND THE MAXIMUM VALUE FOR k4

$$A := k3^2 \quad A = 0 \text{ sec}^2 \cdot \text{nF}^2$$

$$B := 2 \cdot k2 \cdot k3 - 4 \cdot T2 \cdot k1 \cdot k3 \quad B = -1.145 \times 10^{-15} \text{ sec}^2 \cdot \text{nF}$$

$$C := k2^2 - 4 \cdot T2 \cdot k3 \cdot k1 \quad C = 0 \text{ sec}^2 \cdot \text{nF}^2$$

$$k4_{\min} := \frac{-B - \sqrt{B^2 - 4 \cdot A \cdot C}}{2 \cdot A} \quad k4_{\min} = 0.465$$

$$k4_{\max} := \frac{-B + \sqrt{B^2 - 4 \cdot A \cdot C}}{2 \cdot A} \quad k4_{\max} = 1.277 \times 10 \quad (k4 := k4_{\min})$$

NOW SOLVE FOR C1 AND THE OTHER COMPONENTS

$$A := T2 \cdot (k4 + 1) \quad A = 6.234 \times 10^{-6} \text{ sec}$$

$$B := -k2 - k3 \cdot k4 \quad B = -4.235 \times 10^{-5} \text{ sec} \cdot \text{pF}$$

$$C := k3 \cdot k1 \quad C = 7.191 \times 10^{-5} \text{ sec} \cdot \text{pF}^2$$

SOLVE FOR COMPONENTS

$$C1 := \frac{-B}{2 \cdot A} \quad C3 := k4 \cdot C1$$

$$C2 := k1 - C3 - C1 \quad R3 := \frac{k3}{C1 \cdot C3}$$

$$R2 := \frac{T2}{C2}$$

CALCULATIONS USING THE STANDARD METHOD

$$T1 := \frac{\left(\frac{1}{\cos(\phi)} \right) - \tan(\phi)}{\omega c \cdot \left(\frac{T3T1}{100} + 1 \right)}$$

$$T3 := \frac{T3T1}{100} \cdot T1$$

$$T2 := \frac{1}{\left[\omega c^2 \cdot (T1 + T3) \right]}$$

$$C1s := \frac{T1}{T2} \cdot \frac{K\phi \cdot Kvco}{\omega c^2 \cdot N} \cdot \left[\frac{1 + \omega c^2 \cdot T2^2}{(1 + \omega c^2 \cdot T1^2) \cdot (1 + \omega c^2 \cdot T3^2)} \right]^{\frac{1}{2}}$$

$$C2s := C1s \cdot \left(\frac{T2}{T1} - 1 \right)$$

$$C3s := \frac{C1s}{10}$$

$$R2s := \frac{T2}{C2s}$$

$$R3s := \frac{T3}{C3s}$$

ASSIGN COMPONENT VALUES BASED ON USER'S SELECTION OF EITHER THE STANDARD OR ULTIMATE METHOD

C1 := if(method > 0.5, C1, C1s) C3 := if(method > 0.5, C3, C3s) R3 := if(method > 0.5, R3, R3s)

C2 := if(method > 0.5, C2, C2s) R2 := if(method > 0.5, R2, R2s)

THE CALCULATED VALUES ARE SHOWN BELOW

C1 = 3.3961487 pF

C2 = 70.985 pF

C3 = 1.5787196 pF

R2 = 59.9571783 kΩ

R3 = 176.5631365 kΩ

ENTER PARAMETERS HERE

Kφ := Kφ

Fcomp := Fcomp

Fout := Fout

Kvco := Kvco

C1 := C1


R3 := R3

C2 := C2

C3 := C3

R2 := R2

Changes to actual loop filter: C3 := 3pF

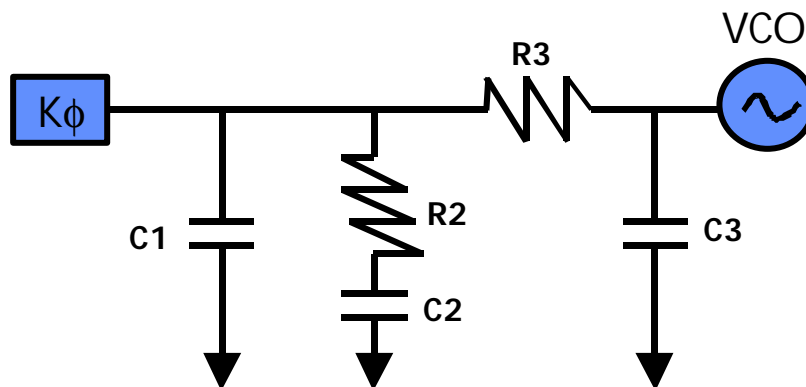

CALCULATE PARAMETERS

$$N := \frac{F_{out}}{F_{comp}}$$

$$\zeta := \frac{R2 \cdot C2}{2} \cdot \sqrt{\frac{K\phi \cdot Kvco}{N \cdot (C1 + C2 + C3)}}$$

$$\omega_n := \sqrt{\frac{K\phi \cdot Kvco}{N \cdot (C1 + C2 + C3)}}$$

$$N = 110$$

$$\zeta = 0.799$$

$$\frac{\omega_n}{2 \cdot \pi} = 59.758 \text{ kHz}$$

CALCULATE THE TRUE POLES AND ZERO

$$T2 := R2 \cdot C2$$

$$x := \frac{C2 \cdot C3 \cdot R2 + C1 \cdot C2 \cdot R2 + C1 \cdot C3 \cdot R3 + C2 \cdot C3 \cdot R3}{C1 + C2 + C3}$$

This is T1+T3

$$y := \frac{R2 \cdot R3 \cdot C1 \cdot C2 \cdot C3}{C1 + C2 + C3}$$

This is T1*T3

$$T1 := \frac{x + \sqrt{x^2 - 4 \cdot y}}{2}$$

$$T3 := \frac{x - \sqrt{x^2 - 4 \cdot y}}{2}$$

junk := T3

Make sure that T1 and T3 are not switched

$$T3 := \text{if}(T3 > T1, T1, T3)$$

$$T1 := \text{if}(T3 > T1, \text{junk}, T1)$$

Time Constant

Filter Pole

Filter Zero

$$T1 = 7.244 \times 10^{-7} \text{ sec}$$

$$\frac{1}{T1} = 1.381 \times 10^3 \text{ kHz}$$

n/a

$$T2 = 4.256 \times 10^{-6} \text{ sec}$$

n/a

$$\frac{1}{T2} = 234.96 \text{ kHz}$$

$$T3 = 1.366 \times 10^{-7} \text{ sec}$$

$$\frac{T3}{T1} = 18.857 \%$$

$$\frac{1}{T3} = 7.321 \times 10^3 \text{ kHz}$$

n/a

DEFINE LOOP PARAMETERS

$$Z(\omega) := \frac{1 + T2 \cdot i \cdot \omega}{i \cdot \omega \cdot (C1 + C2 + C3) \cdot (1 + i \cdot \omega \cdot T1) \cdot (1 + i \cdot \omega \cdot T3)}$$

Loop Filter Impedance

$$G(\omega) := \frac{K\phi \cdot Kvco \cdot Z(\omega)}{i \cdot \omega}$$

Forward Loop Gain

$$CL(\omega) := \frac{G(\omega)}{1 + \frac{G(\omega)}{N}}$$

Closed Loop Gain

BANDWIDTH AND PHASE MARGIN

$$\omega := 600.0 \cdot \text{kHz}$$

Initial Guess for Loop Bandwidth

$$\omega_C := \text{root}(|G(\omega)| - N, \omega)$$

$$\frac{\omega_C}{2 \cdot \pi} = 94.142 \text{ kHz}$$

Loop Bandwidth

$$\omega := \omega_C$$

$$\frac{\text{root}(|CL(\omega)| - N, \omega)}{2 \cdot \pi} = 135.097 \text{ kHz}$$

0 db Bandwidth

$$\frac{\text{root}\left(|CL(\omega)| - \frac{N}{\sqrt{2}}, \omega\right)}{2 \cdot \pi} = 166.638 \text{ kHz}$$

3 db Bandwidth

$$\arg(G(\omega_C)) \cdot \frac{180}{\pi} + 180 = 40.523$$

Phase Margin

ADDED SPURIOUS ATTENUATION (THIRD ORDER FILTERS ONLY)

$$\text{spur}(\omega) := 10 \cdot \log \left[\frac{1 + [\omega_C \cdot (T1 + T3)]^2}{1 + [\omega \cdot (T1 + T3)]^2} \cdot \frac{1 + (\omega \cdot T1)^2}{1 + (\omega_C \cdot T1)^2} \cdot \frac{1 + (\omega \cdot T3)^2}{1 + (\omega_C \cdot T3)^2} \right]$$

$$\text{spur}(2 \cdot \pi \cdot F_{\text{comp}}) = 21.518$$

Additional Reference freq (Fc) Atteunation

$$\text{spur}\left(\frac{1}{4} \cdot 2 \cdot \pi \cdot F_{\text{comp}}\right) = 9.812$$

Attenuation at Fc/4

OPTIMIZATION INDEX (100% = Most Optimized)

$$\text{Index} := \frac{\frac{T2}{1 + (\omega_C \cdot T2)^2}}{\frac{T1}{1 + (\omega_C \cdot T1)^2} + \frac{T3}{1 + (\omega_C \cdot T3)^2}}$$

$$\text{Index} := \text{if} \left(\text{Index} > 1, \frac{1}{\text{Index}}, \text{Index} \right)$$


$$\text{Index} = 77.572\%$$

This is the Optimization Index in Percent

DISPLAY BODE PLOT

$$x := 10 \cdot \text{Hz}, 100 \cdot \text{Hz} .. \frac{10 \cdot \omega_c}{2 \cdot \pi}$$

Open Loop Gain and Phase Margin

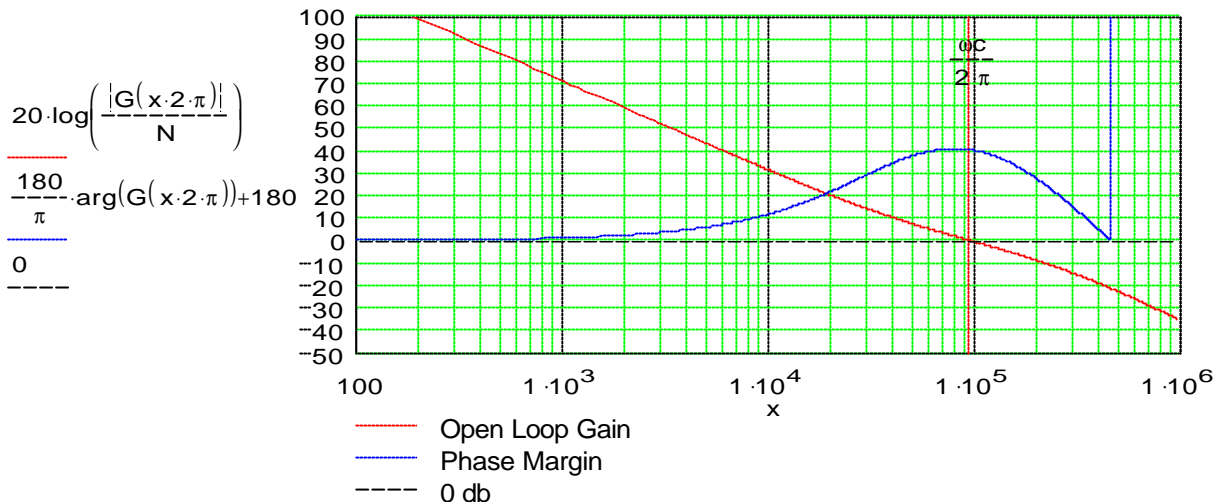

PHASE NOISE PROFILE FOR A NOISELESS VCO

$$\text{Noise1Hz} := -206$$

dbc/Hz

1 Hz Normalized Phase Detector
Phase Noise, max typically -207

$$\text{NoiseFloor} := \text{Noise1Hz} + 10 \cdot \log\left(\frac{F_{\text{comp}}}{\text{Hz}}\right)$$

$$\text{NoiseFloor} = -133.959$$

dbc/Hz

Noise Floor of PLL

$$\text{NoiseFloor} + 20 \cdot \log(N) = -93.131$$


dbc/Hz

In loop Phase Noise

$$\sqrt{\frac{2 \cdot \text{sec}}{\pi}} \int_{10 \cdot \text{Hz}}^{4 \cdot \omega_c} \frac{\text{NoiseFloor}}{10^{10}} \cdot (|CL(\omega)|)^2 d\omega = 1.334 \text{ deg}$$

RMS Phase Error

Phase Noise Profile for Noiseless VCO

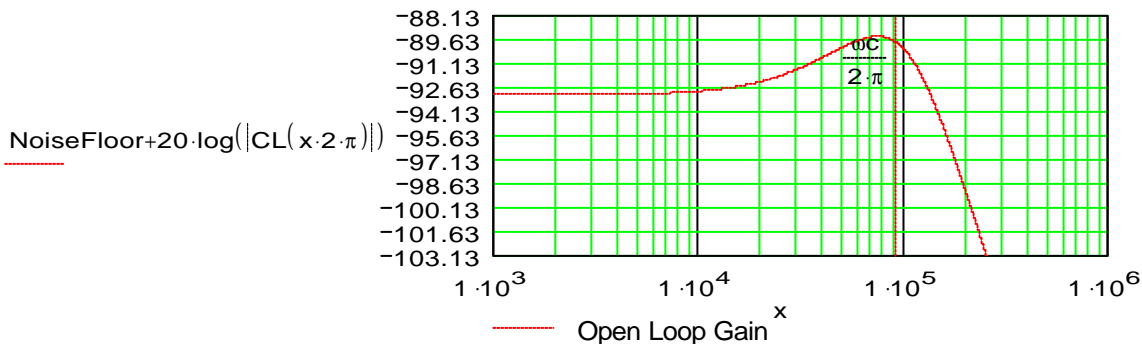

TRANSIENT ANALYSIS

$$f2 := 1760 \cdot \text{MHz} \quad \text{Final Frequency}$$

$$f1 := 1860 \cdot \text{MHz} \quad \text{Starting Frequency}$$

$$R3 := \max\left(\left(\begin{array}{c} R3 \\ 1 \cdot \Omega \end{array}\right)\right) \quad C3 := \max\left(\left(\begin{array}{c} C3 \\ 1 \cdot \text{pF} \end{array}\right)\right)$$

$$N := \frac{f2}{F_{\text{comp}}} \quad \text{den2} := C1 + C2 + C3 \quad \text{den3} := C2 \cdot C3 \cdot R2 + C1 \cdot C2 \cdot R2 + C1 \cdot C3 \cdot R3 + C2 \cdot C3 \cdot R3$$

$$\text{den4} := R2 \cdot R3 \cdot C1 \cdot C2 \cdot C3$$

$$\text{den1} := \frac{K\phi \cdot K_{\text{vco}} \cdot C2 \cdot R2}{N} \quad \text{num0} := \frac{K\phi \cdot K_{\text{vco}} \cdot (f2 - f1)}{N}$$

$$\text{den0} := \frac{K\phi \cdot K_{\text{vco}}}{N} \quad \text{num1} := \text{num0} \cdot R2 \cdot C2$$

$$v := \begin{pmatrix} \frac{\text{den0}}{\text{den4}} \cdot \text{sec}^4 \\ \frac{\text{den1}}{\text{den4}} \cdot \text{sec}^3 \\ \frac{\text{den2}}{\text{den4}} \cdot \text{sec}^2 \\ \frac{\text{den3}}{\text{den4}} \cdot \text{sec} \\ 1 \end{pmatrix} \quad v = \begin{pmatrix} 1.425 \times 10^{24} \\ 6.064 \times 10^{18} \\ 1.011 \times 10^{13} \\ 8.702 \times 10^6 \\ 1 \end{pmatrix}$$

$$p := \text{polyroots}(v) \cdot \text{sec}^{-1} \quad p = \begin{pmatrix} -7.451 \times 10^6 \\ -4.451 \times 10^5 \\ -4.028 \times 10^5 - 5.171i \times 10^5 \\ -4.028 \times 10^5 + 5.171i \times 10^5 \end{pmatrix} \text{sec}^{-1} \quad \text{These are the poles}$$

$$A_0 := \frac{\frac{\text{num0}}{\text{den4}}}{(p_0 - p_1) \cdot (p_0 - p_2) \cdot (p_0 - p_3)} \quad A_0 = 4.072 \times 10^{11} \text{sec}^{-2}$$

$$A_1 := \frac{\frac{\text{num0}}{\text{den4}}}{(p_1 - p_0) \cdot (p_1 - p_2) \cdot (p_1 - p_3)} \quad A_1 = -7.555 \times 10^{13} \text{sec}^{-2}$$

$$A_2 := \frac{\frac{\text{num0}}{\text{den4}}}{(p_2 - p_0) \cdot (p_2 - p_1) \cdot (p_2 - p_3)} \quad A_2 = 3.757 \times 10^{13} - 3.103i \times 10^{11} \text{sec}^{-2}$$

$$A_3 := \frac{\frac{\text{num0}}{\text{den4}}}{(p_3 - p_0) \cdot (p_3 - p_1) \cdot (p_3 - p_2)} \quad A_3 = 3.757 \times 10^{13} + 3.103i \times 10^{11} \text{sec}^{-2}$$

4 Pole Analysis

$k := 0..4000$ $i := 0..3$

$$t_k := \frac{k}{10000000} \cdot \text{sec}$$

$$F(t, k) := f_2 + \sum_i A_i \cdot e^{(p_i \cdot t_k)} \cdot \left(\frac{1}{p_i} + R_2 \cdot C_2 \right)$$

$\text{range} := 100 \cdot 10^{(-6)} \cdot \text{sec}$

Maximum Range of the X axis

$\text{tol} := -0.01 \cdot \text{MHz}$


Tolerance Marker for Lock Time Measurements

$\text{span} := 200 \cdot \text{MHz}$

Vertical Span of the Plot

$\text{center} := 1760 \cdot \text{MHz}$

Center Frequency

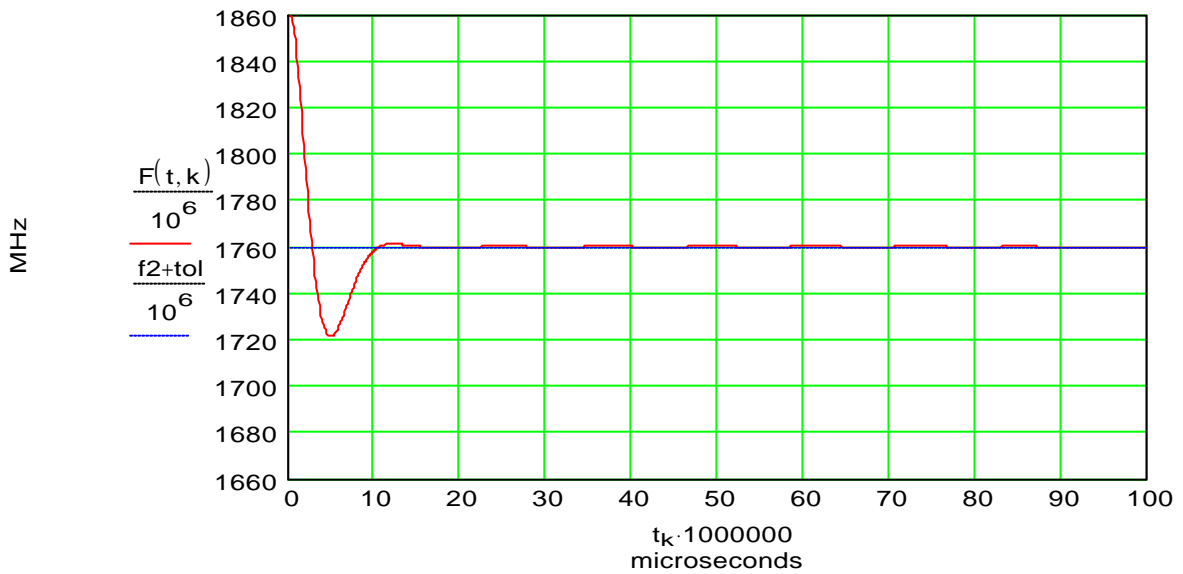

$\text{span} := 0.2 \cdot \text{MHz}$

