

# Values for Discrete Component Branch Line Coupler (Type-2)

Chris Haji-Michael  
<http://www.sunshadow.co.uk/chris.htm>

This page calculates the circuit values for a branch line coupler. The equations are adapted from "Microwave Engineering using Microstrip", Fooks, Zakarevicius, P158. In this coupler the wanted power goes from port 1 to port 2; coupled to port 3.

**Freq := 2.0 · 10<sup>9</sup> Hz**

**c := -2, -4 .. -16** Coupling Ratio (power to port 3 wrt 2)

**Zo := 50ohm**

nH := 1 · 10<sup>-9</sup> H

$$k_2(c) := 10^{\left(\frac{c}{10}\right)} \quad k_3(c) := 1 - k_2(c) \quad k(c) := \frac{k_2(c)}{k_3(c)}$$

$$Z_1(c) := \left(\frac{1}{k(c)^{0.5}}\right) \cdot Z_o \quad Z_2(c) := \left(\frac{1}{k(c) + 1}\right)^{0.5} \cdot Z_o$$

LosstoP2(c) := 10 · log(k3(c))


$$L_1(c) := Z_1(c) \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$L_2(c) := Z_2(c) \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$CL_1(c) := \frac{1}{Z_1(c)} \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$CL_2(c) := \frac{1}{Z_2(c)} \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

C(c) := CL1(c) + CL2(c)

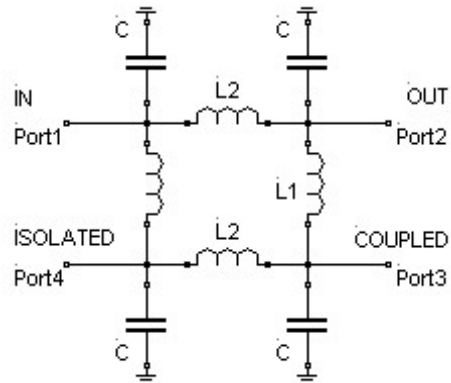

c =	Z1(c) =	ohm	Z2(c) =	ohm
-2	38.24		30.37	
-4	61.48		38.79	
-6	86.33		43.27	
-8	115.21		45.87	
-10	150.00		47.43	
-12	192.67		48.4	
-14	245.55		48.99	
-16	311.49		49.37	

Z1 = port 1 to 4 (shunt)  
 Z2 = port 2 to 3 (series)

c =	L1(c) =	nH	L2(c) =	nH	C(c) =	pF	LosstoP2(c) =
-2	3.04		2.42		4.70		-4.329
-4	4.89		3.09		3.35		-2.205
-6	6.87		3.44		2.76		-1.256
-8	9.17		3.65		2.43		-0.749
-10	11.94		3.77		2.21		-0.458
-12	15.33		3.85		2.06		-0.283
-14	19.54		3.90		1.95		-0.176
-16	24.79		3.93		1.87		-0.110