

## Tuned Three Stage Coaxial Filter

This sheet is used to design **three** coax filters that use semi-rigid RG402 coax cables with capacitors at the bottom to tune.  
Equations are derived from starting point from Pozar "Microwave Engineering" or circuit Sage website. The conversion from ABCD to S21 is from  
Dean Frickley, MTT Feb 1994 "Conversion between S and ABCD valid for complex impedances"

There is no optimisation with this sheet

The filter is tuned using the capacitors

**Chris Haji-Michael**  
<http://www.sunshadow.co.uk/chris.htm>

Where  $Z_{\text{capgnd}}$  is the impedance of the trimming cap to gnd  
 $Z_{\text{tlgnd}}$  is the impedance to gnd of the coax 50 Ohm cable with the capacitor at the bottom end

$$Z_{\text{capgnd}}(\text{freq}, \text{capL}) := -j \cdot \frac{1}{2 \cdot \mathbf{p} \cdot \text{freq} \cdot \text{capL} \cdot \text{ohm}} \quad Z_{\text{tlgnd}}(\text{freq}, \text{freqL}, \text{capL}) := 50 \cdot \frac{Z_{\text{capgnd}}(\text{freq}, \text{capL}) + j \cdot 50 \cdot \tan\left(2 \cdot \mathbf{p} \cdot \frac{\text{freq}}{8 \cdot \text{freqL}}\right)}{50 + j \cdot Z_{\text{capgnd}}(\text{freq}, \text{capL}) \cdot \tan\left(2 \cdot \mathbf{p} \cdot \frac{\text{freq}}{8 \cdot \text{freqL}}\right)}$$

$$Z_{\text{coax}}(\text{freq}, \text{freqL}, \text{capL}) := \begin{pmatrix} 1 & 0 \\ \frac{1}{Z_{\text{tlgnd}}(\text{freq}, \text{freqL}, \text{capL})} & 1 \end{pmatrix} \quad \text{This is the impedance of a 50 Ohm coax cable with capacitors at bottom}$$

$$Z_{\text{cap}}(\text{freq}, \text{cap}) := \begin{pmatrix} 1 & \frac{1}{j \cdot 2 \cdot \mathbf{p} \cdot \text{freq} \cdot \text{cap} \cdot \text{ohm}} \\ 0 & 1 \end{pmatrix} \quad \text{This is the impedance of a series capacitor}$$

This makes ABCD matrix for three coax filter, f1 and f2 are the resonant lengths of the coax cable and S21 is calculated below

$$Z_{2p}(\text{freq}, f1, f2, \text{capL}, \text{cap1}, \text{cap2}) := Z_{\text{cap}}(\text{freq}, \text{cap1}) \cdot Z_{\text{coax}}(\text{freq}, f1, \text{capL}) \cdot Z_{\text{cap}}(\text{freq}, \text{cap2}) \cdot Z_{\text{coax}}(\text{freq}, f2, \text{capL}) \cdot Z_{\text{cap}}(\text{freq}, \text{cap2}) \cdot Z_{\text{coax}}(\text{freq}, f1, \text{capL}) \cdot Z_{\text{cap}}(\text{freq}, \text{cap1})$$

$$R_{\text{load}} := 50 \cdot \text{ohm}$$

$$\log S_{21}(f, f_1, f_2, c_L, c_1, c_2) := 20 \log \left[ \frac{\left( \frac{R_{load}^2}{ohm^2} \right)^{0.5}}{Z_{2p}(f, f_1, f_2, c_L, c_1, c_2)_{0,0} \cdot \frac{R_{load}}{ohm} + Z_{2p}(f, f_1, f_2, c_L, c_1, c_2)_{0,1} + \frac{R_{load}^2}{ohm^2} \cdot Z_{2p}(f, f_1, f_2, c_L, c_1, c_2)_{1,0} + Z_{2p}(f, f_1, f_2, c_L, c_1, c_2)_{1,1} \cdot \frac{R_{load}}{ohm}}, 10 \right]$$



$$c_1 := 2.7pF$$

$$c_2 := 0.82pF$$

$$f_1 := 152MHz$$

$$f_2 := 140MHz$$

$$c_L := 4pF$$

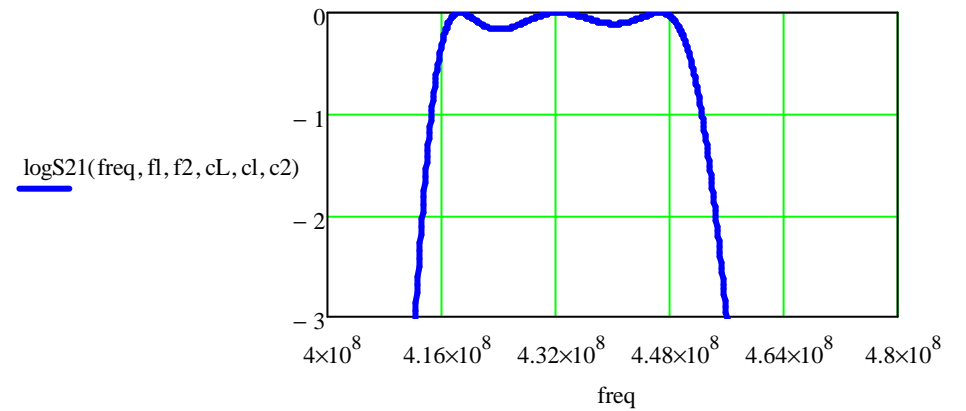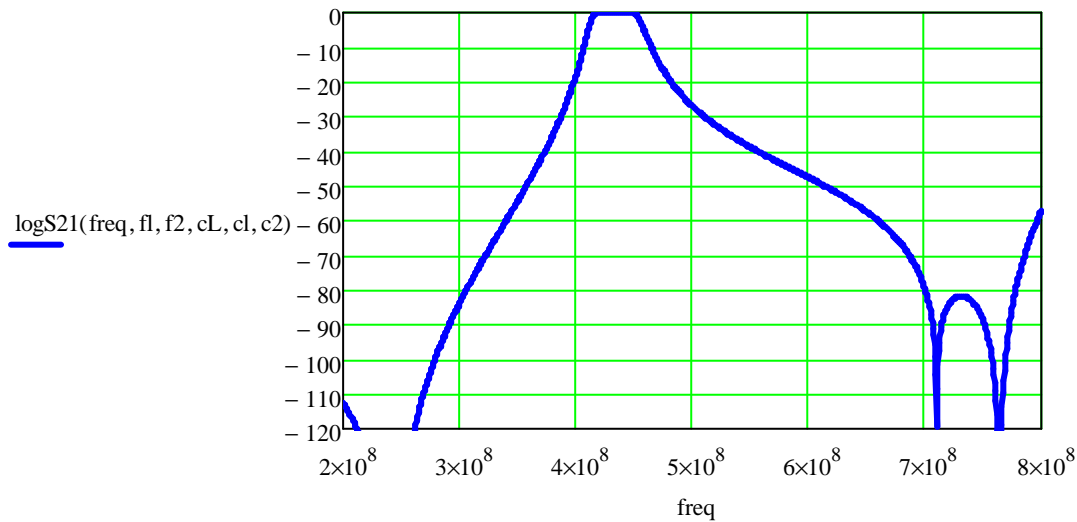


Now we can build the filter using RG402 semi rigid coax cable,  
this equation gets the length

$$\text{inductorlength}(\text{freq}) := \frac{300 \cdot 10^6 \cdot m \cdot s^{-1}}{\text{freq} \cdot 8 \cdot \sqrt{2.1}} - 3mm$$

$$\text{inductorlength}(f_1) = 167.2464 \cdot mm$$
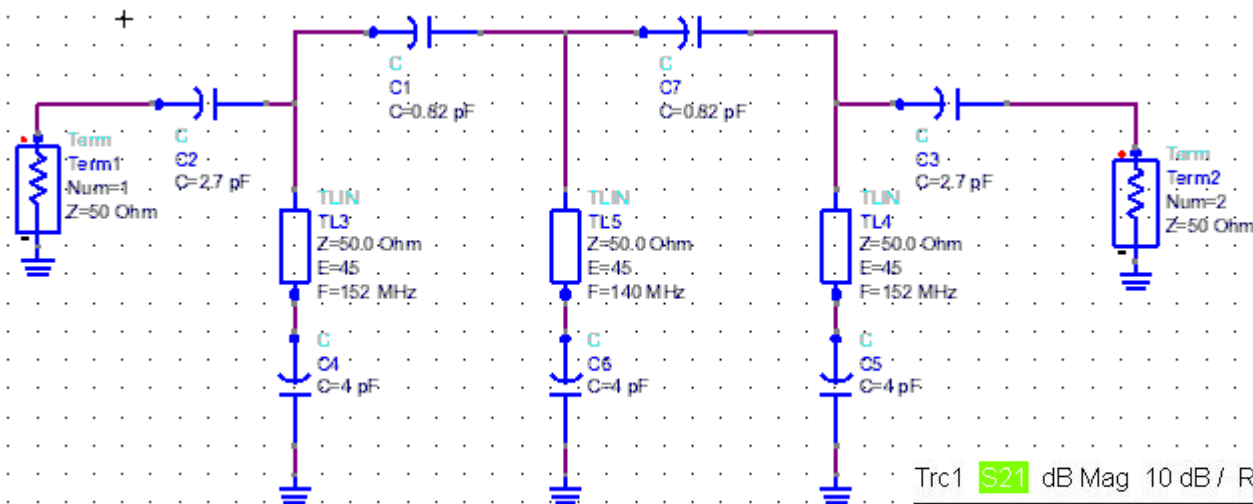
$$\text{inductorlength}(f_2) = 181.839 \cdot mm$$



This is the actual response of filter, marker is at 434MHz, rather good, but the filter is quite large. At least it can be trimmed as cutting the coax cables is not so easy!!!

