

Microwave Coupled Filter Design Sheet



Chris Haji-Michael
www.sunshadow.co.uk/chris.htm

This sheet is used to design microwave Coupled filters. The maths for this can be found at www.acusd.edu/~ekim/e194rfs01/iec19aek.pdf. I have also added some simulation results at the end.

There are three steps to this filter design:

Step 1, Get the filter g-values, this sheet calculated the g values according to the Chebychev polynomial, but these can be obtained in a variety of ways from books or from a program freely available from my web page. You will be pleased to know that these g-values agree with my program!!

Step 2, Calculate Z_{0o}/Z_{0e} and wavelength depending on the type of filter.
This MathCAD sheet stops at this point.

Step 3, Calculate length and width. One method is to use Linecalc which is part of ADS. For microstrip designs I have written a MathCAD sheet which is available from my webpage that works well for thin tracks, less well for thicker tracks. Also you can try transcalc.sourceforge.net for a Linecalc equivalent.

Yellow is user input, Green is output

Main user input area:

$L_{ar_db} := 0.5$

passband ripple in dB

$\mu\text{m} := 10^{-6} \cdot \text{m}$ $\text{nH} := 10^{-9} \cdot \text{henry}$

$N := 5$

order of the filter (this sheet is only valid for odd values of N)

$f_{low} := 10 \cdot \text{GHz}$

bandpass cutoff frequencies, these are the equiripple band edge frequencies, not necessarily the 3 dB cutoff frequencies.

$f_{high} := 15 \cdot \text{GHz}$

$Z_o := 50 \cdot \Omega$

BPF Frequency Response, for Chebychev Polynomials

This section plots the frequency response for the Chebychev polynomial values calculated later. The frequency response is for the coupled BPF.

$$Y_o := \frac{1}{Z_o}$$

$$f_{gm} := \sqrt{f_{low} \cdot f_{high}}$$

$$bw := \frac{f_{high} - f_{low}}{f_{gm}}$$

$$bwpercent := bw \cdot 100$$

$$\mathbf{e} := 10^{\frac{L_{ar_db}}{20}} - 1$$

$$\text{bwpercent} = 40.825$$

$$f_{gm} = 12.247 \cdot \text{GHz}$$

$$\mathbf{e} = 0.122$$

$$L_A(f, f_1) := \begin{cases} 10 \cdot \log \left[1 + \mathbf{e} \cdot \left[\cos \left(\left(N \cdot \arccos \left(\frac{f}{f_1} \right) \right) \right) \right]^2 \right] & \text{if } f \leq f_1 \\ 10 \cdot \log \left[1 + \mathbf{e} \cdot \left[\cosh \left(\left(N \cdot \operatorname{acosh} \left(\frac{f}{f_1} \right) \right) \right) \right]^2 \right] & \text{if } f > f_1 \end{cases}$$



$f_1 = f_c$ for lowpass, f_{gm} for bandpass

$$S11_A(f, f_1) := 10 \cdot \log \left[1 - 10^{\left(\frac{-L_A(f, f_1)}{20} \right)} \right]$$

$$f_{bp}(f) := \frac{1}{bw} \cdot \left(\frac{f}{f_{gm}} - \frac{f_{gm}}{f} \right) \cdot f_{gm}$$

$$f_{bp_narrow} := 0.99 \cdot f_{low}, \frac{f_{high} - f_{low}}{100} + 0.99 \cdot f_{low} .. 1.01 \cdot f_{high}$$
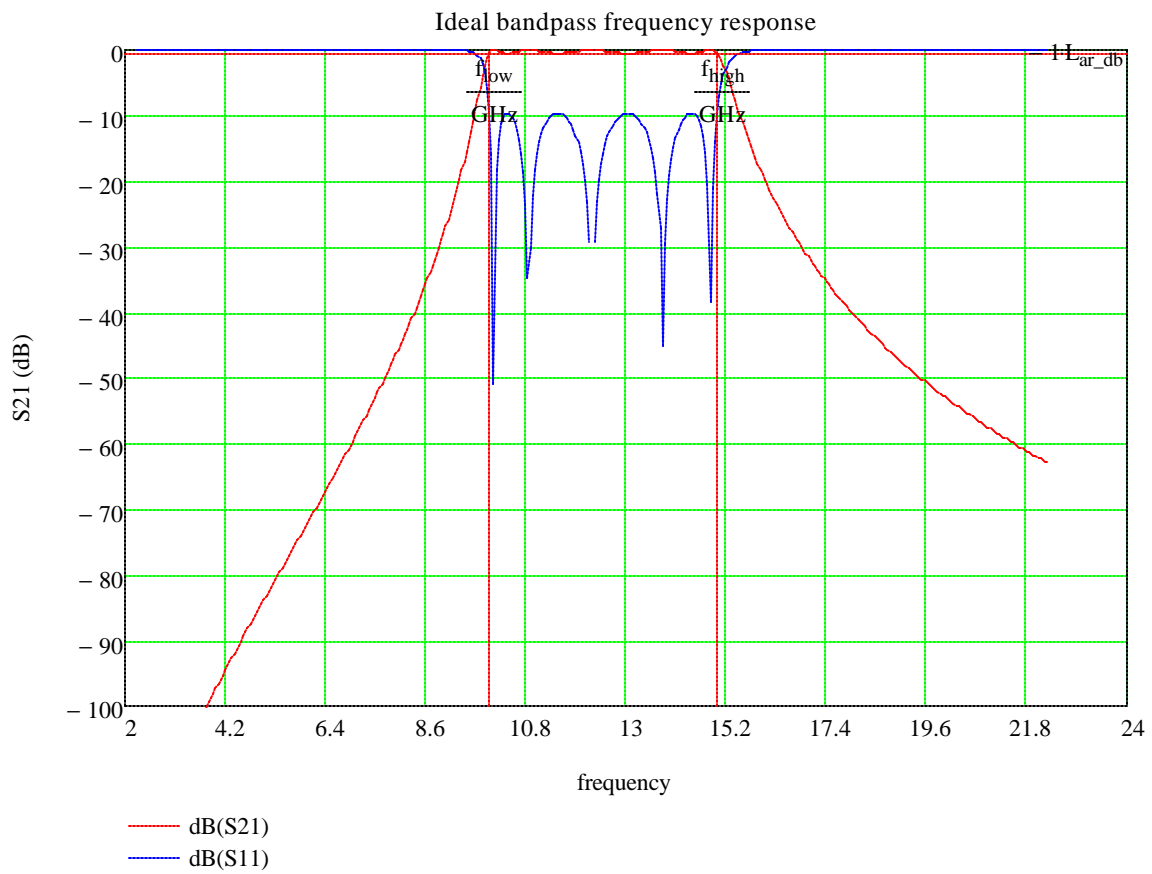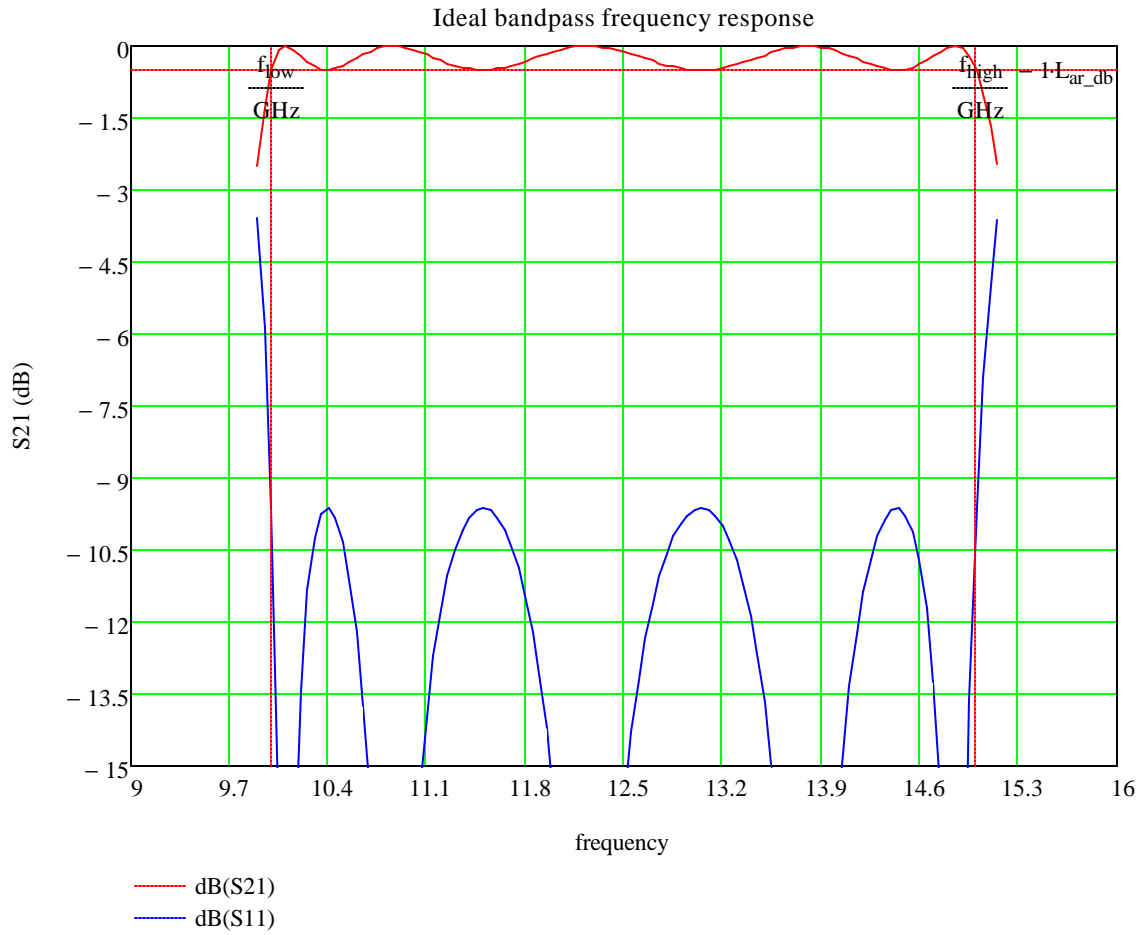
$$f_{bp_wide} := (f_{gm} - 2 \cdot f_{gm} \cdot bw), (f_{gm} - 2 \cdot f_{gm} \cdot bw) + \frac{f_{gm} \cdot bw}{100} .. f_{gm} + (2 \cdot f_{gm} \cdot bw)$$



Calculate the Chebychev (g) Polynomials

$$k := 1..N \quad \mathbf{B} := \ln \left(\coth \left(\frac{L_{ar_db}}{17.37} \right) \right) \quad ? := \sinh \left(\frac{\mathbf{B}}{2 \cdot N} \right) \quad a_k := \sin \left[\frac{(2 \cdot k - 1) \cdot \mathbf{p}}{2 \cdot N} \right]$$

$$b_k := ?^2 + \left(\sin \left(\frac{k \cdot \mathbf{p}}{N} \right) \right)^2 \quad g_k := 0$$

$$g_0 := 1$$

$$g_{N+1} := 1$$

$g(0)$ and $g(N+1)$ represent the input/output coupling for odd order filters, these are 1 representing the generator (and equal) load resistance

$$g_k := \begin{cases} \frac{2 \cdot a_1}{?} & \text{if } k = 1 \\ \frac{4 \cdot a_{k-1} \cdot a_k}{b_{k-1} \cdot g_{k-1}} & \text{otherwise} \end{cases}$$

$$g = \begin{pmatrix} 1 \\ 1.706 \\ 1.23 \\ 2.541 \\ 1.23 \\ 1.706 \\ 1 \end{pmatrix}$$

The next step is to calculate Zoo Zoe.

This next section converts the g-values to J-values and in turn to Zoo and Zoe. If you wish to use your own g-values, i.e not from the Chebychev polynomial then this is ok and you need to put them here as follows.

$$n := 0, 1..N$$

$$g_{100} := 2$$

$$JJ(i) := \begin{cases} \sqrt{\frac{\mathbf{p} \cdot bw}{2 \cdot g_0 \cdot g_1}} & \text{if } i = 0 \\ \frac{\mathbf{p} \cdot bw}{2 \cdot \sqrt{g_i \cdot g_{i+1}}} & \text{if } (1 \leq i < N) \\ \sqrt{\frac{\mathbf{p} \cdot bw}{2 \cdot g_N \cdot g_{N+1}}} & \text{if } i = N \end{cases}$$

$$Jval_n := JJ(n)$$

$$Zoe(n) := \frac{1}{Y_o} \cdot \left[1 + Jval_n + (Jval_n)^2 \right]$$

$$Zoo(n) := \frac{1}{Y_o} \left[\left[1 - Jval_n + (Jval_n)^2 \right] \right]$$

$$Jval = \begin{pmatrix} 0.613 \\ 0.443 \\ 0.363 \\ 0.363 \\ 0.443 \\ 0.613 \end{pmatrix}$$

$$Zoe(n) =$$

$$Zoo(n) =$$

$$\text{coupling_db}(Z_{0e}, Z_{0o}) := 20 \cdot \log\left(\frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}}\right)$$

Now calculate the coupling between sections of the filter. The first and last represent the input and output couplings. If the filter is a tapped filter, the input and output coupling is not achieved using a coupler, and these values are ignored (these are the first and last in the list, and generally represent the smallest coupling value in the filter, which is why it is often desirable to avoid such coupler designs).

$$e_r := 4.5 \quad ?_0 := \frac{3 \cdot 10^8 \cdot \frac{\text{m}}{\text{s}}}{f_{\text{gm}}} \quad ?_{\text{guide}} := \frac{?_0}{\sqrt{e_r}}$$

99.453
81.942
74.721
74.721
81.942
99.453

38.14
37.664
38.441
38.441
37.664
38.14

$$\text{coupling_db}(Z_{0e}(n), Z_{0o}(n)) =$$



-7.021
-8.631
-9.881
-9.881
-8.631
-7.021

$$\frac{?_{\text{guide}}}{4} = 2.887 \cdot \text{mm}$$

length of each quarter wave coupled section

Simulation Results

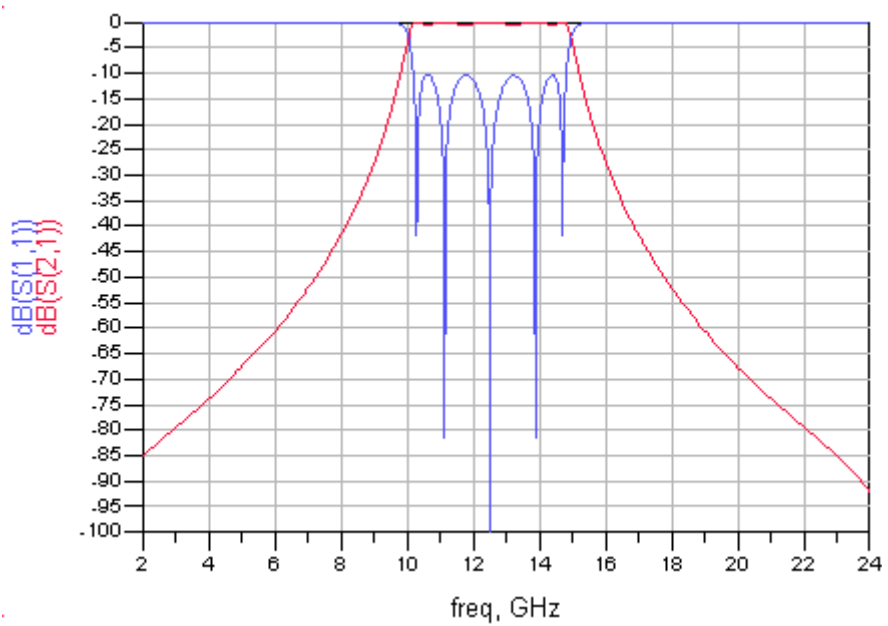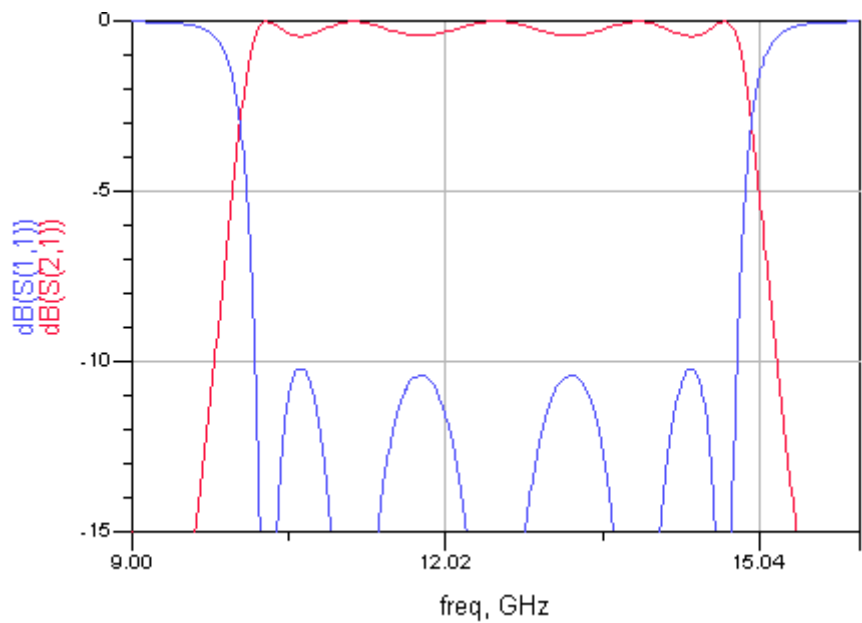To test these values, I have run a simulation on ADS and as you can see the results are in pretty good agreement.



Chebyshev coupled BPF, 0.5dB ripple, N=7

