

Microwave Stepped Impedance Filter Design Sheet

Chris Haji-Michael
www.sunshadow.co.uk/chris.htm



The maths for this can be found at www.acusd.edu/~ekim/e194rfs01/iec19aek.pdf. I have also added some simulation results at the end.

There are three steps to this filter design:

Step 1, Get the filter g-values, this sheet calculated the g values according to the Chebychev polynomial, but these can be obtained in a variety of ways from books or from a program freely available from my web page. You will be pleased to know that these g-values agree with my program!!

Step 2, Calculate Zo and wavelength depending on the type of filter.
This MathCAD sheet stops at this point.

Step 3, Calculate length and width. One method is to use Linecalc which is part of ADS. For microstrip designs I have written a MathCAD sheet which is available from my webpage that works well for thin tracks, less well for thicker tracks. Also you can try transcalc.sourceforge.net for a Linecalc equivalent.

Yellow is user input, Green is output

Main user input area:

$L_{ar_db} := 0.2$ passband ripple in dB $\mu m := 10^{-6} \cdot m$ $nH := 10^{-9} \cdot \text{henry}$

$N := 7$ order of the filter

$f_c := 10 \cdot \text{GHz}$ Cutoff frequency. $Z_o := 50 \cdot \Omega$

LPF Frequency Response, for Chebychev Polynomials

This section plots the frequency response assuming the Chebychev polynomial values calculated later. The frequency response is for the coupled BPF, the LPF response is later.



$$Y_o := \frac{1}{Z_o} \quad e := 10^{\frac{L_{ar_db}}{10} - 1} \quad e = 0.047$$

$$L_A(f, f_1) := \begin{cases} 10 \cdot \log \left[1 + e \cdot \left[\cos \left(\left(N \cdot \arccos \left(\frac{f}{f_1} \right) \right) \right) \right]^2 \right] & \text{if } f \leq f_1 \\ 10 \cdot \log \left[1 + e \cdot \left[\cosh \left(\left(N \cdot \operatorname{acosh} \left(\frac{f}{f_1} \right) \right) \right) \right]^2 \right] & \text{if } f > f_1 \end{cases}$$

$$S11_A(f, f_1) := 10 \cdot \log \left[1 - 10^{\left(\frac{-L_A(f, f_1)}{10} \right)} \right]$$

$$f_{lp_hp_sweep_wide} := \frac{f_c}{10}, \frac{f_c}{10} + \frac{f_c}{50} .. f_c \cdot 5$$
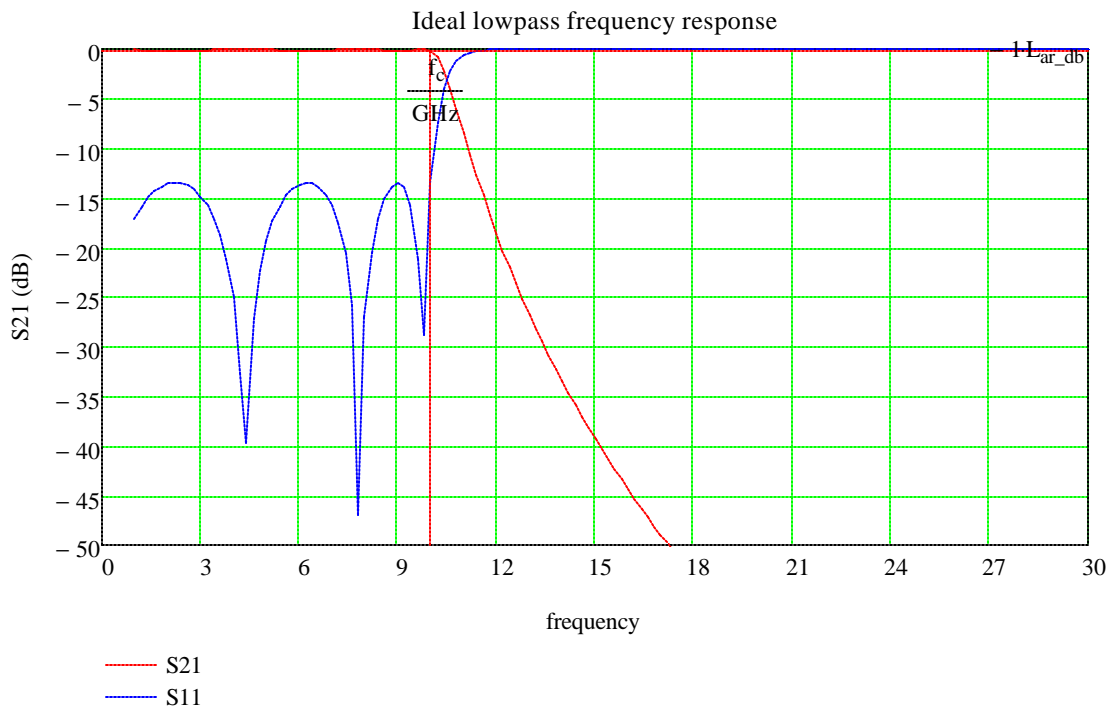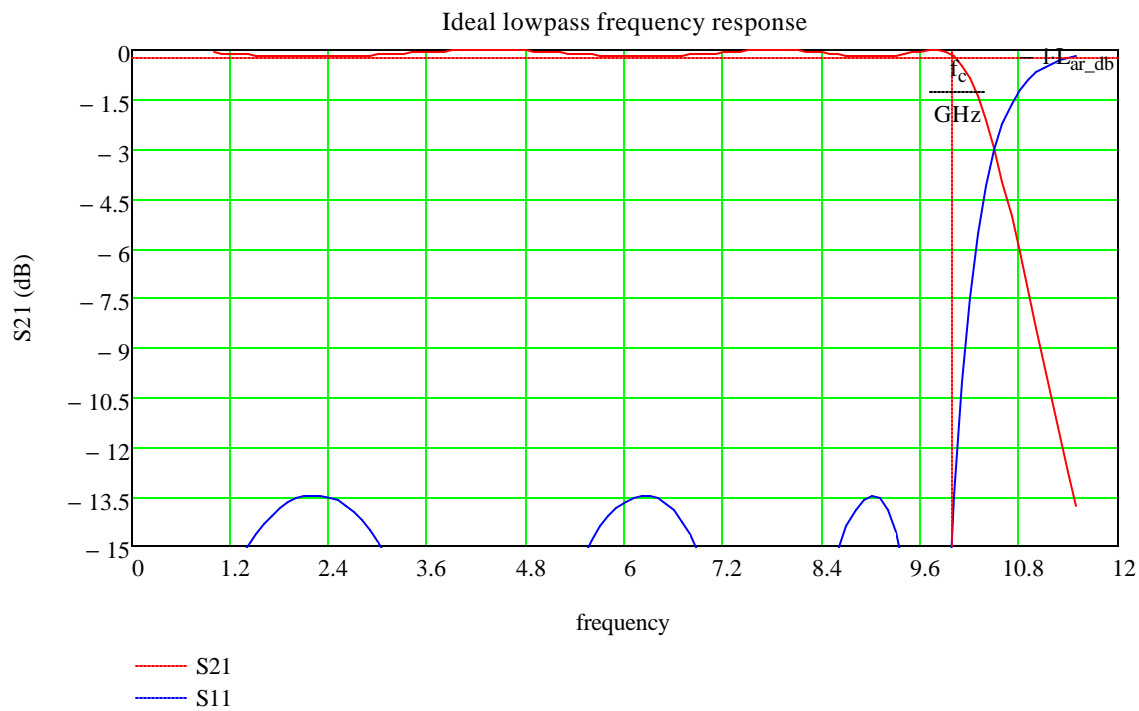
$$f_{lp_hp_sweep_narrow} := \frac{f_c}{10}, \frac{f_c}{10} + \frac{f_c}{100} .. f_c \cdot 1.15$$



Calculate the Chebychev (g) Polynomials

$$k := 1..N \quad \mathbf{B} := \ln \left(\coth \left(\frac{L_{ar_db}}{17.37} \right) \right) \quad ? := \sinh \left(\frac{\mathbf{B}}{2 \cdot N} \right) \quad a_k := \sin \left[\frac{(2 \cdot k - 1) \cdot \mathbf{p}}{2 \cdot N} \right]$$

$$b_k := ?^2 + \left(\sin\left(\frac{k \cdot \mathbf{p}}{N}\right) \right)^2$$

$$g_k := 0$$

$$g_0 := 1$$

$$g_{N+1} := 1$$

$g(0)$ and $g(N+1)$ represent the input/output coupling for odd order filters, these are 1 representing the generator (and equal) load resistance

$$g_k := \begin{cases} \frac{2 \cdot a_1}{?} & \text{if } k = 1 \\ \frac{4 \cdot a_{k-1} \cdot a_k}{b_{k-1} \cdot g_{k-1}} & \text{otherwise} \end{cases}$$

$$g = \begin{pmatrix} 1 \\ 1.372 \\ 1.378 \\ 2.276 \\ 1.5 \\ 2.276 \\ 1.378 \\ 1.372 \\ 1 \end{pmatrix}$$

The next step is to calculate Zo.

This next section converts the g-values to Zo-values. If you wish to use your own g-values, i.e not from the Chebychev polynomial then this is ok and you need to put them here as shown on the right. User sets Zlow and Zhigh based on what is reasonable for the substrate.

This filter alternates between these impedances

$$Z_{low} := 20 \quad Z_{high} := 120$$

$$g_{100} := 2$$

$$\text{angle_L_equiv}_k := \text{asin}\left(\frac{g_k \cdot \frac{Z_o}{\mathbf{O}}}{Z_{high}}\right) \quad \text{angle_C_equiv}_k := \text{asin}\left[\frac{Z_{low}}{\left(\frac{Z_o}{\mathbf{O}}\right)}\right]$$

angle_L_equiv_k =	angle_C_equiv_k =
34.875 · deg	33.293 · deg
35.047	33.455
71.478	65.543
38.687	36.874
71.478	65.543
35.047	33.455
34.875	33.293

There are a number of points to note:

1. The user needs to choose Zhigh/Zlow depending on the substrate.
2. If the angle exceeds 90 degrees then the ripple and N should be changed.
3. For max repeat frequency then the smaller the maximum angle is better.
4. The filter is designed by switching between the inductance/capacitance values in turn, hence two filters are possible from any given results.

Calculate dimensions

Now we can calculate the length of each section.

$$e_r := 4.5 \quad ?_0 := \frac{3 \cdot 10^8 \cdot \frac{m}{s}}{f_c} \quad ? := \frac{?_0}{\sqrt{e_r}}$$

$$? = 14.142 \cdot \text{mm}$$

$$\text{length_L_equiv}_k := ? \cdot \frac{\text{angle_L_equiv}_k}{360 \cdot \text{deg}} \quad \text{length_C_equiv}_k := ? \cdot \frac{\text{angle_C_equiv}_k}{360 \cdot \text{deg}}$$

length_L_equiv _k =		length_C_equiv _k =	
1.37	· mm	1.308	· mm
1.377		1.314	
2.808		2.575	
1.52		1.449	
2.808		2.575	
1.377		1.314	
1.37		1.308	

Simulation Results

To test these values I have run a simulation on ADS and as you can see the results are in good agreement. Both the ripple and return loss (S11) agree, but the cutoff frequency is out and I am not sure why this is. Both types of filter agree with each other.

