

# Transformer Directional Coupler

Chris Haji-Michael

<http://www.sunshadow.co.uk/chris.htm>

This mathcad document is to design a directional coupler using transformers. The equations are from IEE Microwave Antennas and Prop, Vol 14, August 1999. The equations assume tight transformer coupling from 1 to N and are therefore this is only a starting point for a circuit built on a chip.

$$d(N_1, N_2) := 4 \cdot N_1^2 \cdot N_2^2 + 1 + (N_1 - N_2)^2$$

$$S_{11}(N_1, N_2) := \frac{1}{d(N_1, N_2)} \left( -N_1^2 + N_2^2 - 2 \cdot N_1 \cdot N_2 + 1 \right)$$

$$S_{22}(N_1, N_2) := \frac{1}{d(N_1, N_2)} \left( -N_1^2 + N_2^2 + 2 \cdot N_1 \cdot N_2 - 1 \right)$$

$$S_{21}(N_1, N_2) := 20 \cdot \log \left[ \frac{2 \cdot N_1 \cdot N_2}{d(N_1, N_2)} (2 \cdot N_1 \cdot N_2 - 1) \right]$$

$$S_{24}(N_1, N_2) := 20 \cdot \log \left[ \frac{2 \cdot N_1 \cdot N_2}{d(N_1, N_2)} (N_1 + N_2) \right]$$



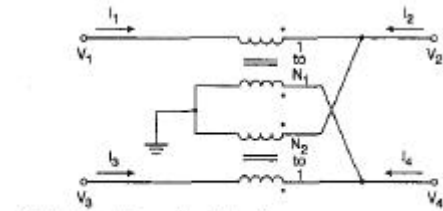
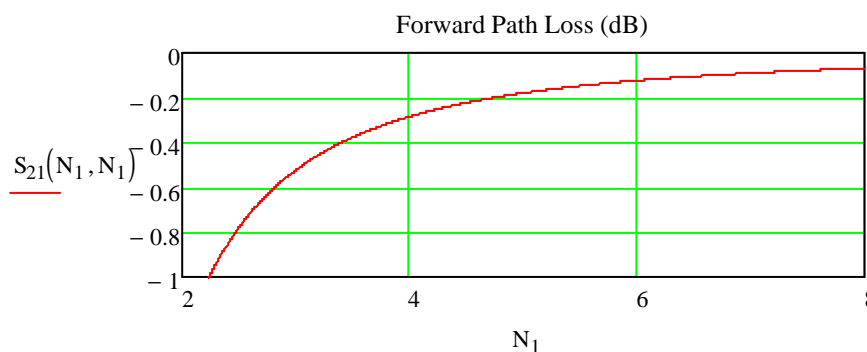


Fig.1 Directional coupler with transformers

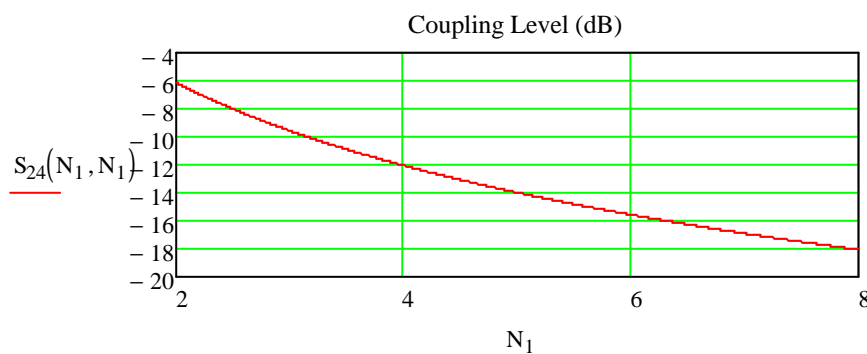

robot Docume

$$VSWR_{in}(N_1, N_2) := \frac{1 + |S_{11}(N_1, N_2)|}{1 - |S_{11}(N_1, N_2)|}$$

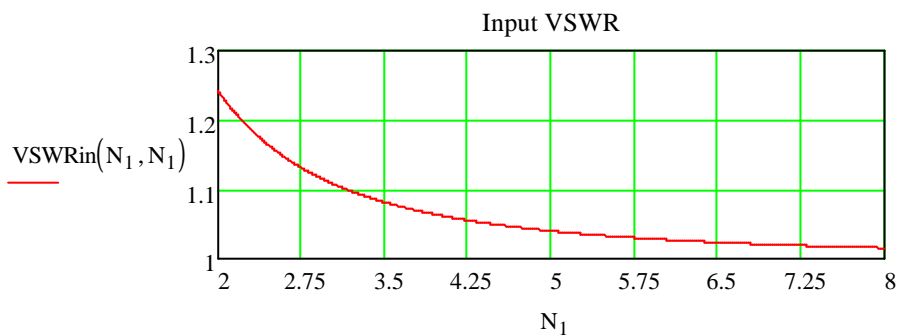


Simulation with N1=2 and N2=6

$$S_{24} = S_{41} = -9.795\text{dB}$$

$$S_{21} = S_{43} = -0.622\text{dB}$$

$$S_{24}(2,6) = -9.795$$

$$S_{21}(2,6) = -0.622$$

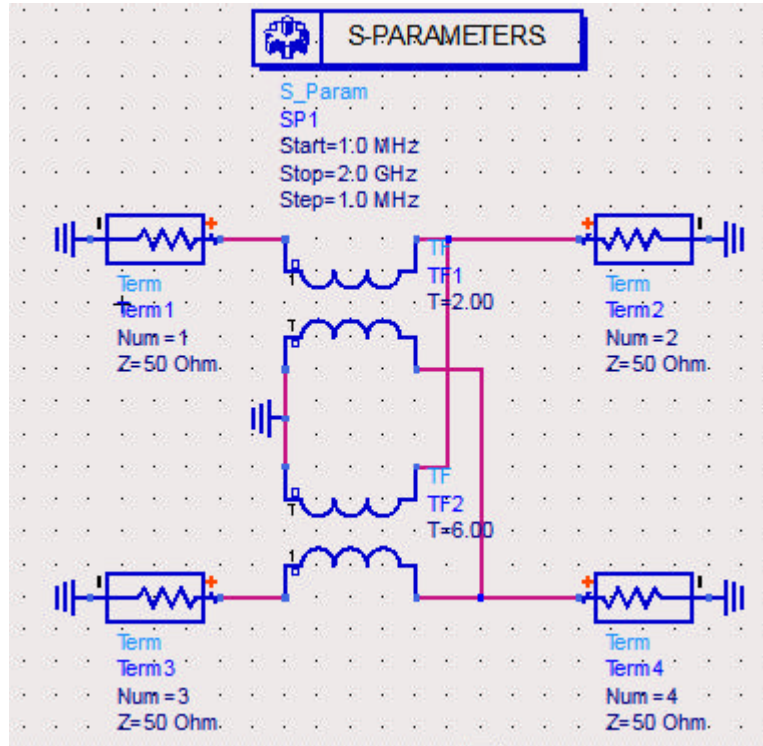

m1  
freq=1.005GHz  
dB(S(3,1))=-9.795

m2  
freq=1.000GHz  
dB(S(2,1))=-0.622

