## **Dual Band, Wilkinson RF Splitter**



## Chris Haji-Michael www.sunshadow.co.uk/chris.htm

This sheet is for a dual-band power-divider.

This is a Wilkinson power splitter that is designed to operate at two frequency bands.

The maths for this filter is from Cheng, Law, IEEE MTT issue 56/2 pages 487 onwards.

Inputs yellow, outputs green

$$\mathbf{\mu}\mathbf{m} \coloneqq 10^{-6} \cdot \mathbf{m} \qquad \mathbf{n}\mathbf{H} \coloneqq 10^{-9} \cdot \mathbf{henry}$$

## Main user input area:

F1 := 1 GHz	F2 := 2.3 GHz	Zo
111012	122.30112	20

z Zo := 50 · ohm



This should be between 1.3 and 2.7

## Calculate:

$$\mathbf{e} := \frac{\mathbf{p}}{2} \cdot \frac{F_1^2}{F_1^2} - 1 \qquad \mathbf{k} := \frac{1 + \sqrt{1 + 8 \cdot (\cot(\mathbf{e}))^2}}{2 \cdot (\cot(\mathbf{e}))^2} \qquad \mathbf{ZA} := \mathbf{Zo} \cdot \sqrt{(1 + \mathbf{k}) \cdot \left[\mathbf{k} - (\tan(\mathbf{e}))^2\right]} \qquad \mathbf{Fo} := \frac{F_2 + F_1}{2}$$

$$\mathbf{R} := 2 \cdot \mathbf{Zo} \cdot \left(1 + \frac{1}{\mathbf{k}}\right) \qquad \mathbf{ZB} := \frac{\mathbf{ZA}}{\mathbf{k}} \qquad \mathbf{ZC} := \frac{\mathbf{ZA}}{\mathbf{k} + (\tan(\mathbf{e}))^2}$$

$Fo = 1.65 \cdot GHz$
$ZA = 67.1 \cdot ohm$
$ZB = 51.9 \cdot ohm$
$ZC = 37.3 \cdot ohm$
$R = 177.4 \cdot ohm$

The S21 and S31 are the same and shown below with 3dB loss each, which is expected. The isolation (S23) is quite interesting as it is more than 20dB down at both operating frequencies. Quite an impressive circuit.



